A UNIFIED FRAMEWORK FOR HARMONIC BALANCE SIMULATION AND SENSITIVITY ANALYSIS


OSA-88-HB-11-V

August 15, 1988

Presented at the Raytheon Company, Lexington, MA, July 14, 1988

A UNIFIED FRAMEWORK FOR HARMONIC BALANCE SIMULATION AND SENSITIVITY ANALYSIS

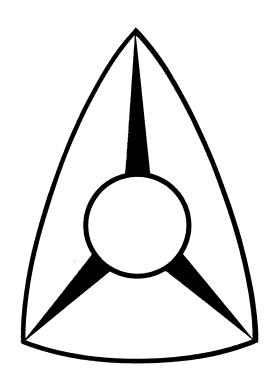Optimization Systems Associates Inc. Dundas, Ontario, Canada



Unified Theoretical Framework

under this framework the following features are unified

simulation and sensitivity analysis

linear and nonlinear circuits

hierarchical and nonhierarchical approaches

voltage and current excitations

open and short circuit terminations

Theoretical Breakthroughs

harmonic balance technique expanded from simulation to adjoint sensitivity analysis

hierarchical approach generalized to permit upward and downward analysis in both the original and adjoint networks

Impact on the Next Generation Circuit CAD

important features of linear simulators, e.g., Super-Compact

syntax-oriented hierarchical approach

design optimization

statistical analysis

yield maximization

these features now applicable to nonlinear circuits

Gradient Optimizers for Circuit CAD

fast convergence

gradient from perturbation

Broyden update formulas

gradients from adjoint network approach

Perturbation Approach to Gradient Evaluation

simulate the circuit to obtain response function f

for i=1, 2, ..., n

perturb the ith variable

simulate the ith perturbed circuit

approximate the derivative of f w.r.t. the ith variable by finite differences

restore the ith variable

Features

n + 1 circuit simulations required

for nonlinear circuits, the starting point for each circuit simulation can be the previous solution; this reduces the number of iterations in nonlinear simulation

Adjoint Network Approach to Gradient Evaluation

for linear circuits

simulate the original circuit to obtain branch voltages V_b simulate the adjoint network to obtain adjoint branch voltages, $\overset{\wedge}{V_b}$ compute sensitivity expressions at element level G_b response sensitivity is typically the algebraic operation of $\overset{\wedge}{V_b}$, $\overset{\wedge}{V_b}$ and G_b

we have extended this approach to nonlinear circuits

Features

extremely fast as compared with the perturbation approach

cost of solving the adjoint network is almost free compared with the cost of simulating the original circuit

adjoint network simulation only solves a set of linear equations

original network simulation solves nonlinear equations using iterative methods

all relevant matrices for the adjoint network equations are already preprocessed, i.e., inverse or LU factors are available and reusable

Notation

V(k) contains <u>external voltages</u> of a linear subcircuit at harmonic k


V_t(k) contains <u>both internal and external voltages</u> of a linear subcircuit at harmonic k

 \overline{V} contains real and imaginary parts of V(k) for all harmonics

denotes adjoint quantities, e.g., V(k)

current vectors I(k), $I_t(k)$, \overline{I} and I(k) similarly defined

Harmonic Balance Simulation

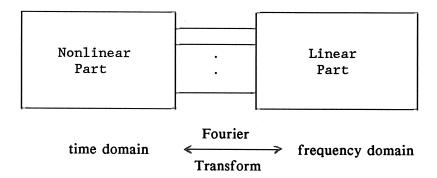

harmonic balance equation

$$\overline{\mathbf{F}}(\overline{\mathbf{V}}) \stackrel{\triangle}{=} \overline{\mathbf{I}}_{\mathrm{NL}}(\overline{\mathbf{V}}) + \overline{\mathbf{I}}_{\mathrm{L}}(\overline{\mathbf{V}}) = \mathbf{0}$$

where $\overline{I}_{NL}(\overline{V})$ and $\overline{I}_{L}(\overline{V})$ represent currents from the linear and the nonlinear parts, respectively

Sensitivity Analysis

sensitivity of output response Vout w.r.t. design variable x

$$\frac{\partial V_{out}}{\partial x}$$

essential for gradient optimizers

Hierarchical Analysis

UPWARD analysis is to obtain the overall circuit matrix, e.g., Y matrix, for the linear part

DOWNWARD analysis is to obtain responses for the linear part at individual components, e.g., voltage or power for an element

TOP LEVEL analysis is to solve the harmonic balance equations for nonlinear networks

TOP LEVEL analysis is to solve the terminated circuit for linear networks

Top Level Simulation of Nonlinear Circuits

harmonic balance equation

$$\overline{\mathbf{F}}(\overline{\mathbf{V}}) = \mathbf{0}$$

Newton update

$$\overline{\mathbf{V}}_{\text{new}} = \overline{\mathbf{V}}_{\text{old}} - \overline{\mathbf{J}}^{-1} \overline{\mathbf{F}} (\overline{\mathbf{V}}_{\text{old}})$$

 \overline{J} is the Jacobian matrix

the Newton solution provides the top level voltages V(k)

Downward Simulation of the Original Linear Network

consider a typical subcircuit

internal and external voltages $V_t(k)$ of the subcircuit can be computed from its external voltages V(k) by

$$\mathbf{A}(\mathbf{k}) \left[\begin{array}{c} \mathbf{V}_{\mathbf{t}}(\mathbf{k}) \\ \mathbf{I}(\mathbf{k}) \end{array} \right] = \left[\begin{array}{c} \mathbf{0} \\ \mathbf{V}(\mathbf{k}) \end{array} \right]$$

A(k) is the modified nodal admittance matrix of the subcircuit

I(k) contains currents into the subcircuit from its external ports

 $V_t(k)$, along with I(k), is a solution to the subcircuit

Implementation

suppose subcircuits C1, C2 and C3 are directly connected to the subcircuit under consideration from below

then solution $V_t(k)$ contains internal and external voltages of the subcircuit under consideration

 $V_t(k)$ also provides external voltages of the lower level subcircuits C1, C2, C3

the equation is used iteratively down the hierarchy until all desired voltages are found

Top Level Adjoint Simulation for Nonlinear Networks

suppose the second entry of $\overline{\mathbf{V}}$ is selected as the output voltage

$$\overline{V}_{\text{out}} = [0\ 1\ 0\ 0\ ..\ 0\]\overline{V}$$

the corresponding adjoint system is

$$\overline{\mathbf{J}}^{\mathsf{T}} \overline{\mathbf{V}} = \begin{bmatrix} 0 \\ 1 \\ 0 \\ . \\ . \\ 0 \\ 0 \end{bmatrix}$$

in the adjoint system, the RHS is the output voltage selection vector whose second entry is 1 and all other entries are 0

the matrix $\overline{\mathbf{J}}$ is the Jacobian matrix previously used in the Newton iteration

the LU factors of \overline{J} available and reusable

the solution gives the top level external adjoint voltages V(k)

Adjoint Voltages when Output Port is Suppressed

disconnect nonlinear part

solve linear part for individual harmonics

 $\frac{\Delta}{V_L}$ contains adjoint voltages at the external ports of the linear subnetwork

adjoint excitations of the overall circuit

$$\overline{\mathbf{J}}^{\mathsf{T}} \overline{\mathbf{V}} = \overline{\mathbf{Y}}^{\mathsf{T}} \overline{\mathbf{V}}_{\mathbf{L}}$$

Downward Simulation of the Adjoint Linear Network

consider a typical subcircuit

internal and external adjoint voltages $V_t(k)$ of the subcircuit can be computed from its external adjoint voltages $V_t(k)$ by

$$\mathbf{A}^{\mathbf{T}}(\mathbf{k}) \begin{bmatrix} \mathbf{\hat{V}}_{t}(\mathbf{k}) \\ \mathbf{\hat{\Lambda}} \\ -\mathbf{I}(\mathbf{k}) \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{\hat{\Lambda}} \\ -\mathbf{\hat{V}}(\mathbf{k}) \end{bmatrix}$$

matrix A(k) is the modified nodal admittance matrix previously used in downward simulation of the original circuit

I(k) contains adjoint currents into the subnetwork from its external ports A $V_t(k)$, along with I(k), is a solution to the adjoint subcircuit

Implementation

solution $V_t(k)$ contains internal and external adjoint voltages of the subnetwork

 $V_t(k)$ also provides external adjoint voltages for downward analysis the LU factors of A(k) are available and reusable

Sensitivity Expressions

variable x belongs to branch b

$$\frac{\partial \overline{V}_{out}}{\partial x} = \begin{cases} -\sum_{k} \text{Real } [V_b(k)V_b^*(k)G_b^*(k)] & \text{(a)} \\ k & \\ -\sum_{k} \text{Real } [V_b(k)G_b^*(k)] & \text{(b)} \\ k & \\ -\sum_{k} \text{Imag } [V_b(k)G_b^*(k)] & \text{(c)} \end{cases}$$

 $V_b(k)$ and $V_b(k)$ are voltages of branch b at harmonic k

G_b(k) is the sensitivity expression at the element level

Examples of G_b(k)

for a linear resistor $G_b(k)=1$

for a nonlinear resistor described by i(t)=i(v(t), x)

 $G_b(k)=[kth Fourier coefficient of \partial i/\partial x]$

Formula vs. Identity of Variables

equation (a) is used if x belongs to the linear part of the circuit

equation (b) is used if x belongs to nonlinear resistive elements, nonlinear voltage controlled current sources or the real part of a complex driving source

equation (c) is used if x belongs to nonlinear capacitive elements or the imaginary part of a complex driving source

SENSITIVITY EXPRESSIONS AT THE ELEMENT LEVEL

Type of Element*	Expression for $G_b(k)$	Applicable Equation	
linear conductor G	1	(a)	
linear resistor R	$-1/R^2$	(a)	
linear capacitor C	$\mathtt{j}\omega_{\mathtt{k}}$	(a)	
linear inductor L	$-1/(j\omega_k L^2)$	(a)	
nonlinear VCCS or nonlinear resistor described by i = i(v(t),x)	[kth Fourier coefficient of $\partial i/\partial x$]	(b)	
nonlinear capacitor described by q = q(v(t),x)	$\omega_{\mathbf{k}}$ [kth Fourier coefficient of $\partial \mathbf{q}/\partial \mathbf{x}$]	(c)	
current driving source	1	(b) or (c) ⁺	
voltage driving source	1/(source impedance)	(b) or (c) ⁺	

 $^{^*}$ the element is located in branch b and contains the variable x.

 $^{^{\}dagger}$ (b) is used if x is the real part of the driving source.

⁽c) is used if x is the imaginary part of the driving source.

 $[\]omega_{\boldsymbol{k}}$ is the kth harmonic frequency used in the harmonic equation.

FET Mixer Example of Camacho-Penalosa and Aitchison (1987)

compute exact sensitivities of the conversion gain w.r.t. 26 variables

all parameters in the linear and nonlinear parts

DC bias, LO power, RF power,

IF, LO and RF terminations

results in excellent agreement with those from perturbation

CPU time for simulation only is 22 seconds on a VAX 8600

CPU time for sensitivity computation

our approach 3.7 seconds

perturbation approach 240 seconds

GRADIENTS OF MIXER CONVERSION GAIN

Variable x	Gradient Expression	
RF power	c Real{ $(\partial V_{out}/\partial x)/V_{out}$ } - 1	
$R_g(f_{RF})$	c Real{ $(\partial V_{out}/\partial x)/V_{out}$ } + c/ $(2R_g(f_{RF}))$	
$R_d(f_{IF})$	c Real($(\partial V_{out}/\partial x)/V_{out}$	
	$-1/(R_d(f_{IF}) + jX_d(f_{IF}))$ + c/(2R _d (f _{IF}))	
$X_d(f_{IF})$	c Real{($\partial V_{\text{out}}/\partial x$)/ V_{out}	
	$- j/(R_d(f_{IF}) + jX_d(f_{IF})) $	
any parameter other than above	c Real{ $(\partial V_{out}/\partial x)/V_{out}$ }	

c = 20/ln10

R and X represent the real and the imaginary parts of the impedance terminations, respectively. Subscripts g and d represent the gate and the drain terminations, respectively.



NUMERICAL VERIFICATION OF SENSITIVITIES OF THE MIXER

Location of Variables	Variable	Exact Sensitivity	Numerical Sensitivity	Difference (%)
linear	C _{ds}	2.23080	2.23042	0.02
subnetwork	C_{gd}	-29.44595	-29.44659	0.00
	C _{de}	0.00000	0.00000	0.03
	R_{g}	3.17234	3.17214	0.01
	R_d	6.42682	6.42751	0.01
	R_s	11.50766	11.50805	0.00
	R _{de}	-0.02396	-0.02412	0.66
	${\tt L_g}$	-0.50245	-0.50346	0.20
	L_d	-0.20664	-0.20679	0.07
	${\tt L_s}$	1.15334	1.15333	0.00
nonlinear	C _{gs0}	-6.17770	-6.17786	0.00
subnetwork*	τ	0.49428	0.49414	0.03
	V_{ϕ}	-20.85730	-20.85758	0.00
	V_{p0}	-26.48210	-26.48041	0.01
	V_{dss}	0.01064	0.01028	3.33
	I _{dsp}	9.93696	9.93680	0.00
bias and	V_{GS}	-31.62080	-31.62423	0.01
driving	v_{DS}	-2.17821	-2.17823	0.00
sources	P_{LO}	2.76412	2.76412	0.00
	P_{RF}	-0.05401	-0.05392	0.16

NUMERICAL VERIFICATION OF SENSITIVITIES OF THE MIXER (continued)

Location of Variables	Variable	Exact Sensitivity	Numerical Sensitivity	Difference (%)
termina- tions	$R_{g}(f_{LO})$	0.06671	0.06657	0.22
	$X_{g}(f_{LO})$	0.37855	0.37854	0.00
	$R_{g}(f_{RF})$	0.78812	0.78798	0.02
	$X_{g}(f_{RF})$	0.45120	0.45119	0.00
	$R_d(f_{IF})$	0.71451	0.71436	0.02
	$X_d(f_{IF})$	0.10886	0.10871	0.14

Nonlinear elements are characterized by

$$C_{gs}(v_1) = C_{gs0} / \sqrt{1-v_1/V_{\phi}},$$

$$R_{i}(v_{1})C_{gs}(v_{1}) = \tau$$

and the function for $i_m(v_1, v_2)$ is shown in the I-V curve of the FET device, whose mathematical expression is consistent with Camacho-Penalosa and Aitchison (1987). V_{\emptyset} , V_{p0} , V_{dss} and I_{dsp} are parameters in the function $i_m(v_1, v_2)$.

Comparison with the Perturbation Method

perturbation method

simulate the original nonlinear circuit

perturb all variables and resimulate for each perturbation

our method

simulate the original circuit

solve the adjoint equations once

features of our method

adjoint simulation noniterative

exact gradient

computation speed fast

Conclusions

unified theory for

simulation and sensitivity analysis

linear and nonlinear circuits

hierarchical and nonhierarchical

since nonlinear simulation is costly, the adjoint sensitivity approach is very significant

our hierarchical approach permits

voltages anywhere in the original and adjoint networks

variables anywhere in the entire circuit

a key for the coming generation of microwave CAD software

Application to Nonlinear Parameter Extraction

operate the device under large signal AC conditions

perform measurements at DC, fundamental as well as higher harmonics

optimize all parameters such that the computed large signal responses match the measured responses at DC, fundamental and all higher harmonics simultaneously

powerful l_1 gradient optimizer should be used

the error function and its derivatives w.r.t. optimization variables are provided by appropriate simulation and sensitivity analysis

Simulation and Sensitivity Analysis for Nonlinear Parameter Extraction

formulate the harmonic balance equations

solve harmonic balance equations, retaining LU factors of the Jacobian matrix at the solution

compute error functions for optimization

define the vector for selecting accessible measurement ports, e.g., drain port

solve the adjoint system using the voltage selection vector as the RHS and the transposed Jacobian as the adjoint network matrix


use downward simulation to obtain all necessary branch voltages (both original and adjoint)

compute (adjoint) sensitivity at element level


compute circuit response sensitivity using our novel formulas

compute gradient vector for optimization



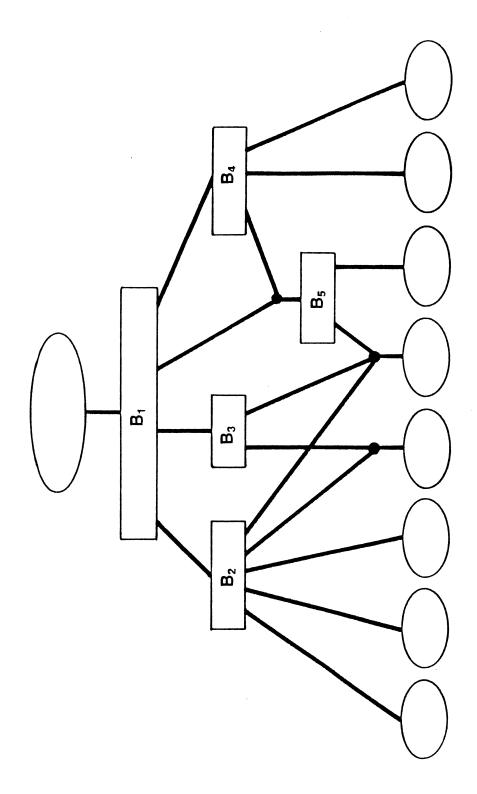

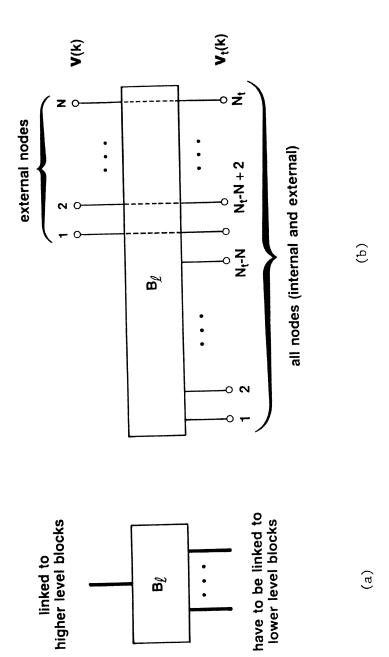An arbitrary circuit hierarchy. Each thick line represents a group of nodes. Each rectangular box represents a connection block for a subcircuit. Each bottom circular box represents a circuit element and the top circular box represents the sources and loads. Fig. 1



A typical subcircuit connection block: (a) as seen from Fig. 1, (b) detailed representation of all the nodes of the subnetwork. Nodes at the top (bottom) of the rectangular box are the external (external and internal) nodes of the subnetwork. Fig. 2


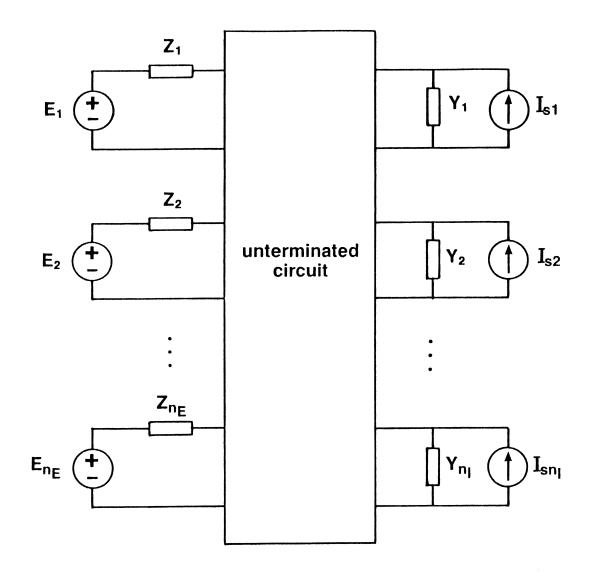


Fig. 3 A representation of a terminated subnetwork. Both current and voltage sources can be accommodated. The overall port sequence is such that ports 1, 2, ..., n_E correspond to voltage sources and ports $n_{E}+1$, $n_{E}+2$, ..., $n_{E}+n_{I}$ correspond to current sources. The total number of ports is N, i.e., $N = n_{E}+n_{I}$.

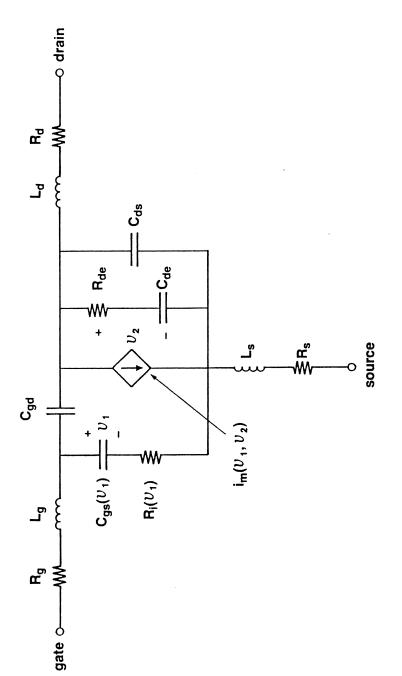



A large signal MESFET model. All parameters are consistent with Camacho-Penalosa and Aitchison (1987). Fig.4

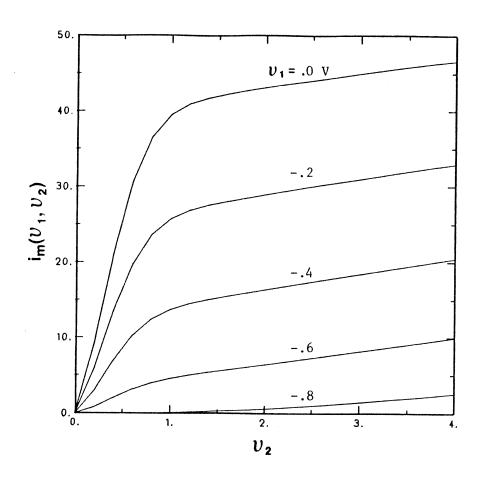


Fig. 5 The DC characteristics of the MESFET model.

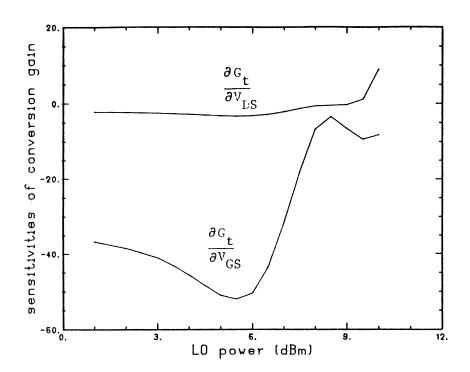


Fig. 6 Sensitivities of conversion gain w.r.t. bias voltages as functions of LO power.