NONLINEAR ANALYSIS OF A CLASS B FREQUENCY DOUBLER

OSA-94-OS-4-R

March 23, 1994

[©] Optimization Systems Associates Inc. 1994



Introduction

A class B frequency doubler is the second CAD benchmark example provided by *Microwave Engineering Europe* for large-signal simulation. The problem statement was received by fax from the Editor on February 24 and on March 1, 1994. It was augmented by a missing data item on March 7, with another data item corrected on March 23. We used HarPE [1], OSA90/hope [2] and Sonnet's *em* [3] to carry out modeling of the NE71000 FET and nonlinear analysis of the doubler.

A. FET Parameter Extraction

Since no large-signal model of the FET was provided by the editor, nor it was available from the manufacturer, we used HarPE to perform parameter extraction to create the large-signal FET model. The data that we utilized for parameter extraction contain typical DC characteristics and typical S parameters from 2 GHz to 26 GHz with 1 GHz step at two bias points published in the "NEC California Eastern Laboratories, RF and microwave Semiconductors" data book [4]. The built-in Curtice and Ettenberg model together with the Extrinsic4 linear subcircuit is chosen to model the FET. The parameter extraction is performed by fitting simultaneously the DC curves at 12 points, and the S parameters at the two bias points and 25 frequencies. Very good DC match and reasonable S-parameter match are obtained.

B. Nonlinear Harmonic Balance simulation

We use OSA90/hope to carry out the nonlinear harmonic balance (HB) simulation of the overall circuit with various component simulations, as summarized by the following three cases.

<u>Case I</u>: All microstrip components are simulated using OSA90/hope's built-in models. This naturally does not include couplings between the components.

<u>Case II</u>: The third harmonic stubs situated at the gate and drain ports of the FET are simulated by *em* [3]. This reflects the coupling between the two stubs.

Case III: In addition to the third harmonic stubs, the bias pads together with the radial stubs are also simulated by em [3]. This reflects the couplings in the biasing subcircuit as well as between the third harmonic stubs.



The conversion gain is calculated by

conversion gain = output power at the second harmonic / available input power.

Results for Case I:

In this case we simulate the circuit by considering all the microstrip elements as independent elements. We use OSA90/hope's built-in microstrip empirical models for all transmission lines, stubs, pads and discontinuities. This approach neglects any couplings between the components, in particular the third harmonic stubs situated at the gate and drain ports of the FET and the bias pads.

The output power and conversion gain versus input power at 7 GHz are shown in Figs. 1 and 2, respectively. The output power and conversion gain versus frequency at 9 dBm input power are shown in Figs. 3 and 4, respectively. A 3D view of conversion gain versus frequency and input power is given in Fig. 5. The source and output voltage waveforms at 7 GHz and 9 dBm input power are plotted in Fig. 6.

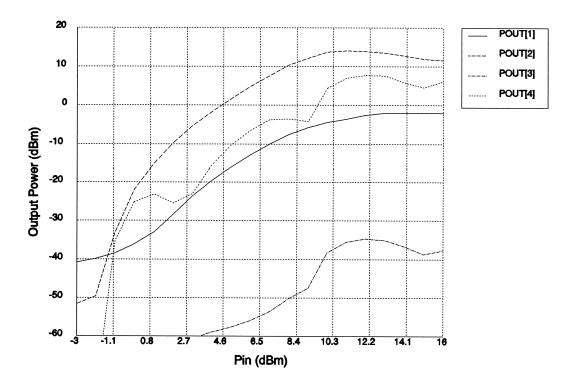


Fig. 1 Output power versus input power at 7 GHz. Couplings are not taken into account.



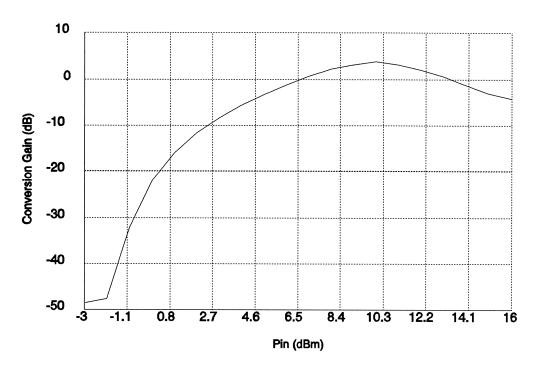


Fig. 2 Conversion gain versus input power at 7 GHz. Couplings are not taken into account.

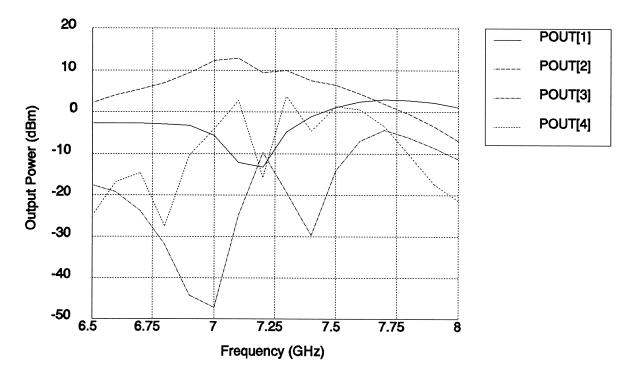


Fig. 3 Output power versus frequency at 9 dBm input power. Couplings are not taken into account.



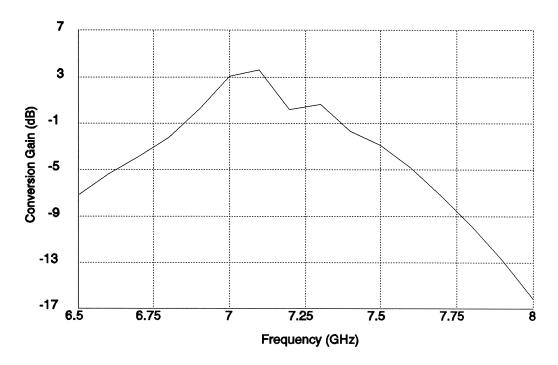


Fig. 4 Conversion gain versus frequency at 9 dBm input power. Couplings are not taken into account.

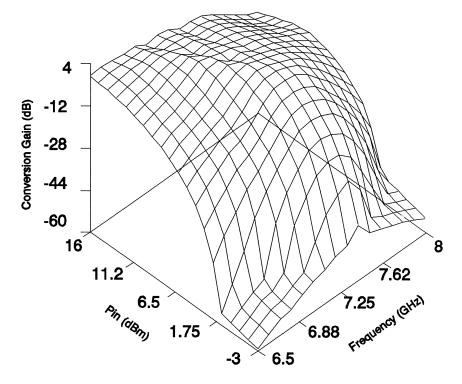


Fig. 5 3D view of conversion gain versus input power and frequency. Couplings are not taken into account.



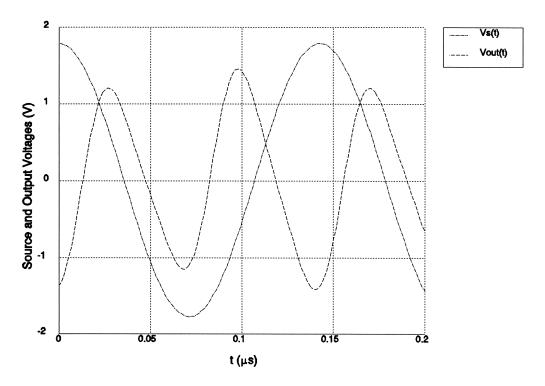


Fig. 6 Source and output voltage waveforms at 7 GHz and 9 dBm input power. Couplings are not taken into account.

Results for Case II:

In this case we consider the coupling effect of the third harmonic stubs situated at the gate and drain ports of the FET. Both stubs are considered as one four-port element which is simulated by *em* [3] and imported to OSA90/hope for circuit-level simulation.

The output power and conversion gain versus input power at 7 GHz are shown in Figs. 7 and 8, respectively. The output power and conversion gain versus frequency at 9 dBm input power are shown in Figs. 9 and 10, respectively. A 3D view of conversion gain versus frequency and input power is given in Fig. 11. The source and output voltage waveforms at 7 GHz and 9 dBm input power are plotted in Fig. 12.



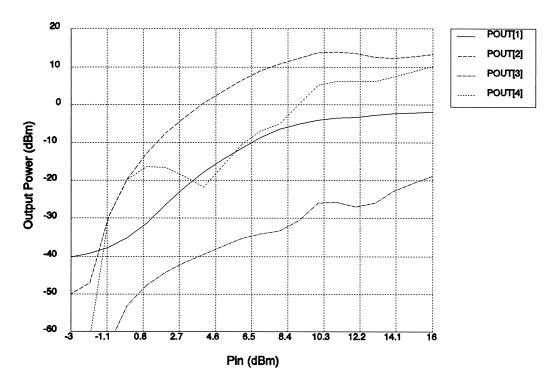


Fig. 7 Output power versus input power at 7 GHz. The coupling between the third harmonic stubs is simulated by *em* [3].

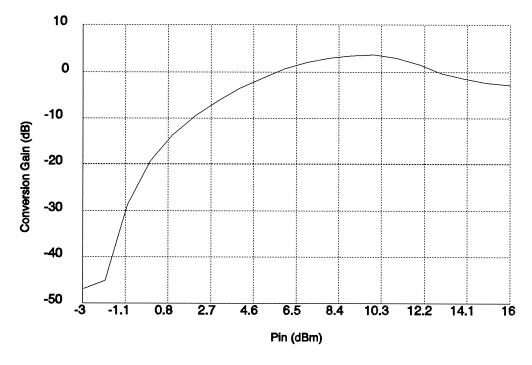


Fig. 8 Conversion gain versus input power at 7 GHz. The coupling between the third harmonic stubs is simulated by *em* [3].



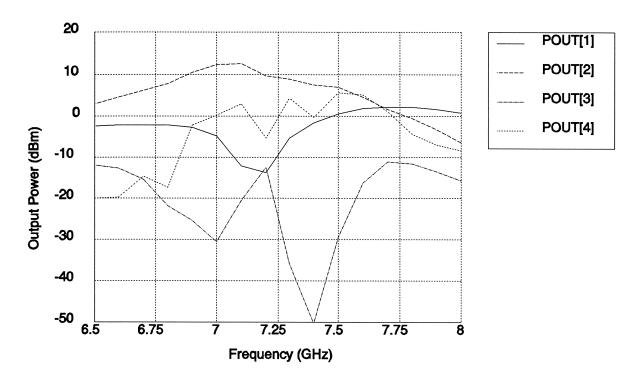


Fig. 9 Output power versus frequency at 9 dBm input power. The coupling between the third harmonic stubs is simulated by *em* [3].

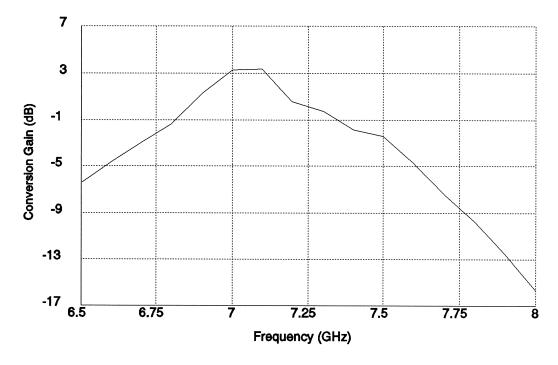


Fig. 10 Conversion gain versus frequency at 9 dBm input power. The coupling between the third harmonic stubs is simulated by *em* [3].



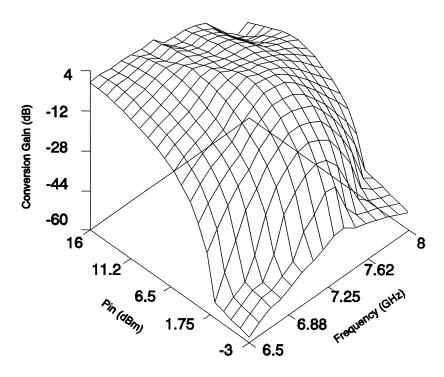


Fig. 11 3D view of conversion gain versus input power and frequency. The coupling between the third harmonic stubs is simulated by *em* [3].

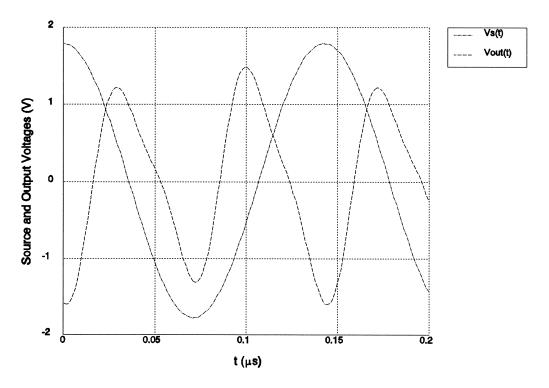


Fig. 12 Source and output voltage waveforms at 7 GHz and 9 dBm input power. The coupling between the third harmonic stubs is simulated by *em* [3].



Comparing Fig. 7 with Fig. 4 we can see that the output power at the third and fourth harmonics at 7 GHz of Case II are higher than those of Case I. Due to the coupling effect the resulting output waveform is slightly more distorted, as seen by comparing Figs. 6 and 12.

Results for Case III:

In this case we consider both the coupling of the third harmonic stubs situated at the gate and drain ports of the FET and the effect of the bias pads. In addition to the third harmonic stubs, each bias pad together with the adjacent radial stub is also simulated by em [3] as a two-port. These three subcircuits are simulated by em [3] and imported into OSA90/hope for overall circuit-level simulation. This reflects the couplings within those three subcircuits (the third harmonic stubs, the gate biasing circuit, and the drain biasing circuit).

The output power and conversion gain versus input power at 7 GHz are shown in Figs. 13 and 14, respectively. The output power and conversion gain versus frequency at 9 dBm input power are shown in Figs. 15 and 16, respectively. A 3D view of conversion gain versus frequency and input power is given in Fig. 17. The source and output voltage waveforms at 7 GHz and 9 dBm input power are plotted in Fig. 18.

Comparing the results of this case with those of Case I and Case II, we can see that the effect of couplings between the bias pads and the radial stubs is quite significant. The output waveform is significantly distorted as seen from Fig. 18.



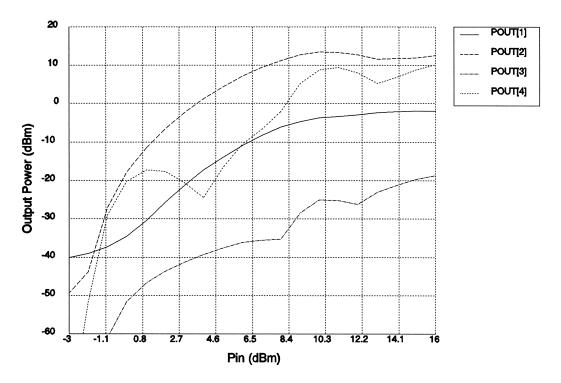


Fig. 13 Output power versus input power at 7 GHz. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

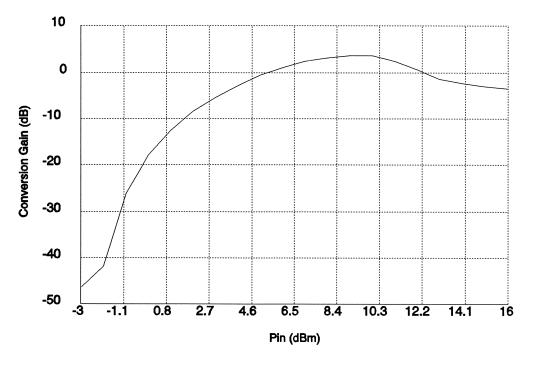


Fig. 14 Conversion gain versus input power at 7 GHz. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].



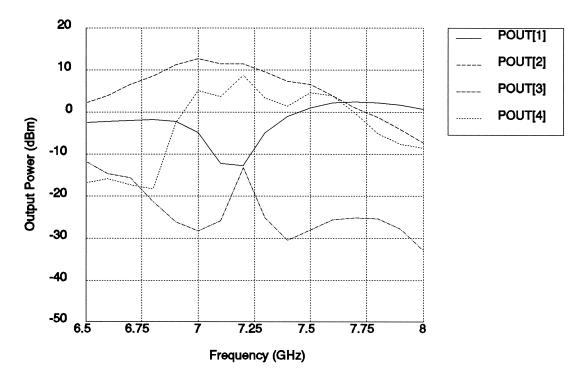


Fig. 15 Output power versus frequency at 9 dBm input power. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

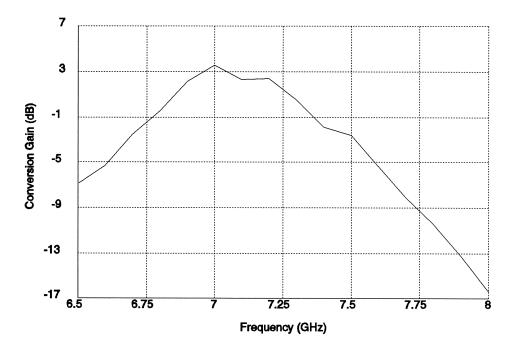


Fig. 16 Conversion gain versus frequency at 9 dBm input power. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].



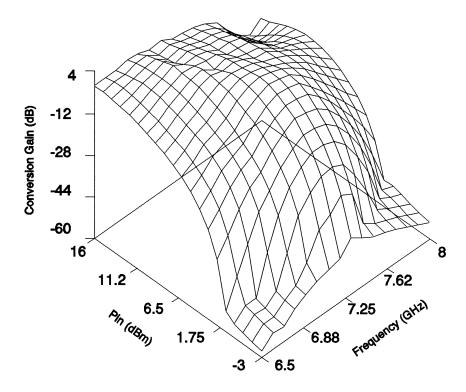


Fig. 17 3D view of conversion gain versus input power and frequency. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

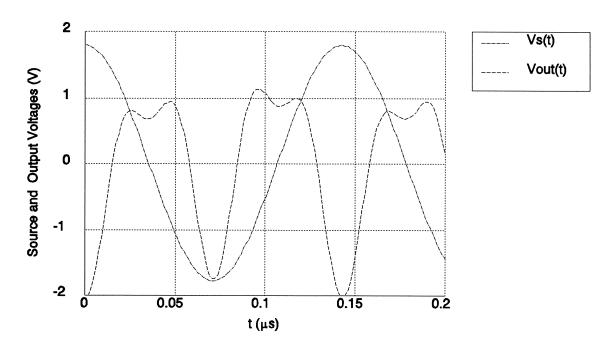


Fig. 18 Input and output voltage waveforms at 7 GHz and 9 dBm input power. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].



C. Statistical Analysis

To investigate the effect of the FET model uncertainty on the simulation result of the circuit, we perform statistical Monte Carlo analysis by assigning tolerances to the model parameters. A uniform distribution with 20 % tolerance is assigned to all model parameters. Monte Carlo analysis with OSA90/hope's built-in microstrip component models (as in Case I) is carried out using 50 outcomes.

The Monte Carlo sweep of the conversion gain versus input power at 7 GHz is shown in Fig. 19. The conversion gain at 7 GHz and 9 dBm input power are spread between -2.4 dB and 4.7 dB. This reflects the model uncertainty and is illustrated by the histogram shown in Fig. 20. 20 % tolerance is quite large, particularly when the parameters are statistically independent. This means that this estimate of the gain spread is fairly pessimistic. In other words, the effect of doubling the frequency is not very sensitive to the transistor parameters, though the spectral purity of the output waveform may be.

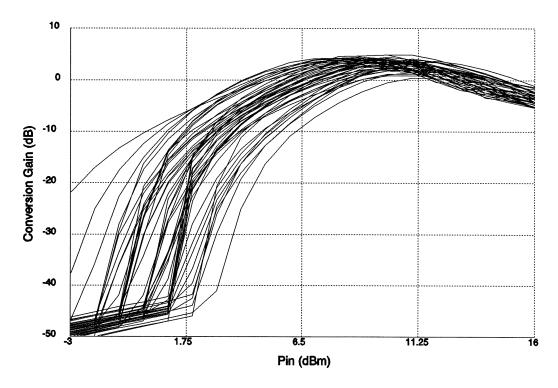


Fig. 19 Monte Carlo sweep of conversion gain versus input power at 7 GHz. Couplings are not taken into account.



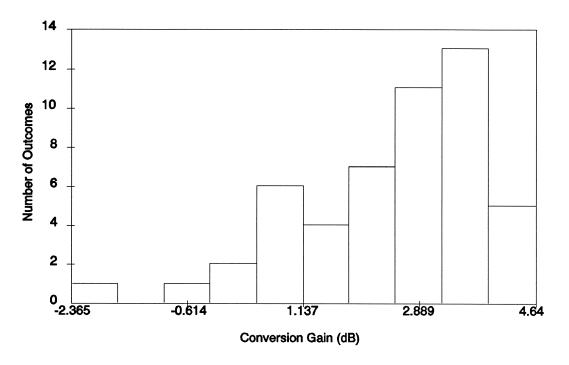


Fig. 20 Histogram of conversion gain at 7 GHz and 9 dBm input power. Couplings are not taken into account.

D. Circuit Optimization

In order to improve the responses of the doubler we use OSA90/hope to optimize the circuit.

The specifications for optimization are

conversion gain > 3 dB spectral purity > 20 dB

at 7 GHz and 9 dBm input power. The spectral purity is calculated by

spectral purity =
$$P_2 / (P_1 + P_3 + P_4)$$

where P_i is the output power at the *i*th harmonic.

The optimization is performed based on the situation of Case III where both the coupling of the third harmonic stubs situated at the gate and drain ports of the FET and the effect of the bias pads are considered. A total of 15 variables are selected for optimization as indicated in Fig. 21.



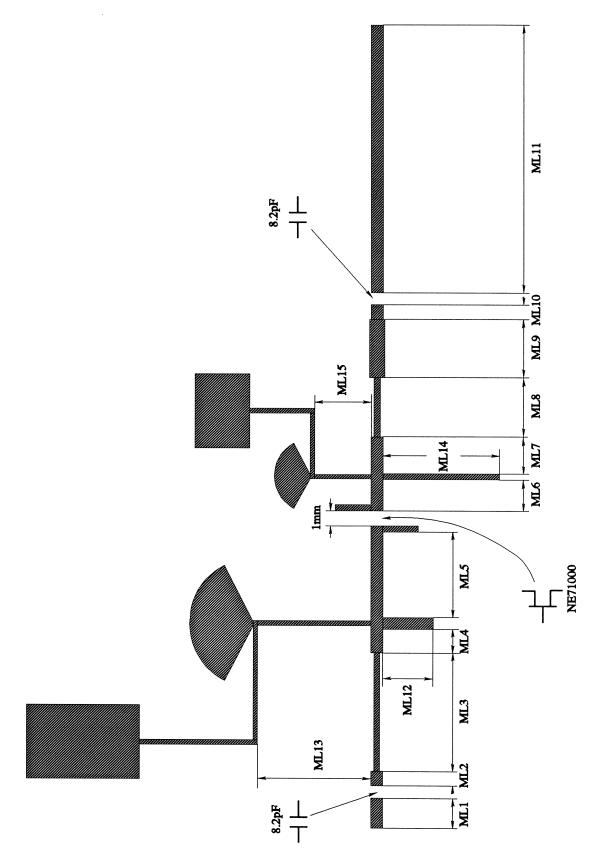


Fig. 21 The doubler circuit and optimization variables.



The minimax optimizer of OSA90/hope is used for this circuit optimization. All specifications are satisfied after optimization. The values of the variables before and after optimization are listed in Table I.

TABLE I
VARIABLE VALUES BEFORE AND AFTER OPTIMIZATION

Variable	Before Optimization	After Optimization
ML1	2.0	1.691
ML2	1.0	0.901
ML3	7.95	6.792
ML4	1.55	1.759
ML5	5.75	5.182
ML6	2.11 + 0.38	1.601 + 0.38
ML7	2.5	2.842
ML8	3.99	3.903
ML9	3.87	3.698
ML10	1	0.994
ML11	20	17.35
ML12	3.395	4.500
ML13	7.68	7.510
ML14	7.85	7.903
ML15	3.82	3.804

All dimensions are in mm.

From Table I we can see that the most influencing variables are ML3, ML11 and ML12. The output power and conversion gain versus input power at 7 GHz are shown in Figs. 22 and 23, respectively. The output power and conversion gain versus frequency at 9 dBm input power are shown in Figs. 24 and 25, respectively. A 3D view of conversion gain versus frequency and input power is given in Fig. 26. The input and output voltage waveforms at 7 GHz and 9 dBm input power are plotted in Fig. 27.

Comparing Figs. 22-27 with Figs. 13-18 we can see that better circuit performance is achieved after circuit optimization.



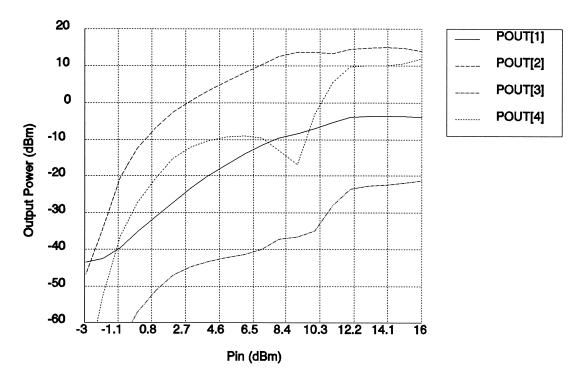


Fig. 22 Output power versus input power at 7 GHz after optimization. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

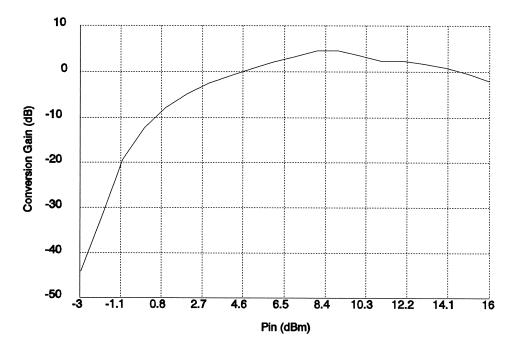


Fig. 23 Conversion gain versus input power at 7 GHz after optimization. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].



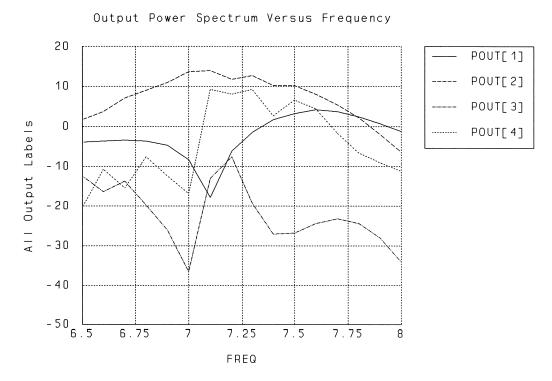


Fig. 24 Output power versus frequency at 9 dBm input power after optimization. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

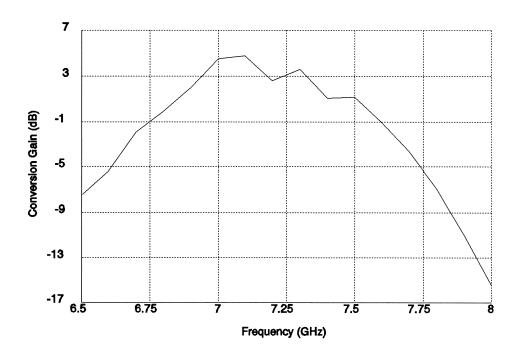


Fig. 25 Conversion gain versus frequency at 9 dBm input power after optimization. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].



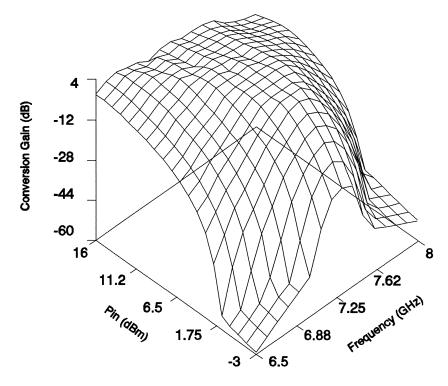


Fig. 26 3D view of conversion gain after optimization. The couplings between the third harmonic stubs and between the bias pads and the corresponding radial stubs are simulated by *em* [3].

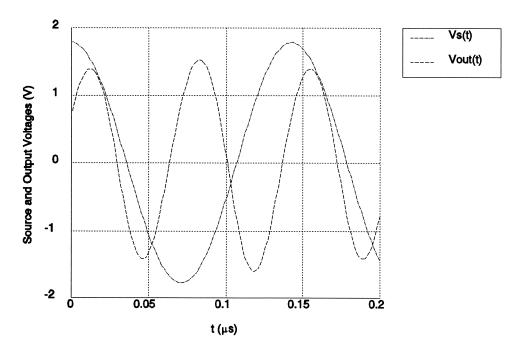


Fig. 27 Source and output voltages at 7 GHz and 9 dBm input power after optimization. The couplings between the third harmonic stubs and between the bias pads and the radial stubs are simulated by *em* [3].



E. Simulation Time

All the experiments reported here were carried out on a Sun SPARCstation 10 workstation. The total time for simulating the complete circuit in Case I with the OSA90/hope built-in models for all the elements including the FET and distributed elements at 320 points (frequency: from 6.5 GHz to 8 GHz with 0.1 GHz step, input power: from -3 dBm to 16 dBm with 1 dBm step) is 1 minute and 45 seconds, about 0.3 second per point.

F. References

- [1] HarPE[™], Optimization Systems Associates Inc., P.O. Box 8083, Dundas, Ontario, Canada L9H 5E7, 1993.
- [2] OSA90/hope[™], Optimization Systems Associates Inc., P.O. Box 8083, Dundas, Ontario, Canada L9H 5E7, 1993.
- [3] Em Version 2.4, Sonnet Software, Inc., Suite 203, 135 Old Cove Road, Liverpool, NY 13090-3774, 1993.
- [4] "RF and Microwave Semiconductors," NEC Data Book, California Eastern Laboratories, 1994.



Appendix: The Circuit File for Case I

```
! dbl c31.ckt
! Simulation of a Class B frequency doubler
! CAD benchmark example provided by Microwave Engineering Europe
! Model used: built-in Curtice and Ettenberg model extracted by HarPE
! The coupling between the 2 stubs at gate and drain and the effect
! of bias pads are not considered
! All the distributed elements are modelled by OSA90/hope's built-in models
  MSUB EPSR=2.2 H=0.254mm T=0.0178mm ROC=2.44e-8 RHS=0.001mm;
  MSL
                W=0.76mm
                          L=2.0mm;
  CAP
         2.
            3
                C=8.2pf;
  MSL
                W=0.76mm
                           L=1.0mm:
  MSTEP
        4
                W1=0.76mm W2=0.4mm:
  MSL
         5
             6
                ₩=0.4mm
                           L=7.95mm;
  MSTEP 6
                W1=0.4mm
                          W2=0.76mm;
  MST.
            8
               W≔0.76mm
                           L=1.55mm;
  MCROSS 10
            8 9 11 W1=0.76mm W2=0.76mm W3=0.3mm;
        11 12 W=0.76mm L=5.75mm;
  MSL
         12 13 14 W1=0.76mm W2=0.38mm W3=0.76mm;
  MTEE
         15
            16 17 W1=0.76mm W2=0.38mm W3=0.76mm;
  MSL
         17
            18 W=0.76mm L=2.11mm;
  MCROSS 20 18 21 19 W1=0.38mm W2=0.76mm W3=0.3mm;
  MST.
         19
            22 W=0.76mm L=2.5mm:
        22
  MSTEP
            23
                W1=0.76mm W2=0.38mm;
  MSI.
         23
            24 W=0.38mm L=3.99mm:
  MSTEP 24 25 W1=0.38mm W2=1.04mm;
  MSL
         25 26 W=1.04mm
                          L=3.87mm:
  MSTEP 26 27 W1=1.04mm W2=0.76mm;
         27 28 W=0.76mm
  MSL
                          L=1mm;
         28 29 C=8.2pf;
  CAP
  MSL
         29
            30 W=0.76mm
                          L=20mm;
         10 31 W=0.76mm
  MSL
                          L=3.395mm:
  OPEN
        31;
  MSL
         13 32 W=0.38mm
                          L=2.4mm;
  OPEN
         32;
  MSL
         16 42 W=0.38mm
                          L=2.4mm;
         42;
  OPEN
  MSL
         20 33 W=0.38mm
                          L=7.85mm;
  OPEN
         33;
  MSL
         9
            34 W=0.3mm
                          L=7.68mm;
  MTEE
         34
            35 36 W1=0.3mm W2=0.3mm W3=0.3mm;
  MSL.
         36
            37
                ₩=0.3mm
                          L=7.68mm;
  MBEND2 37
            38 W=0.3mm;
         38 39 W=0.3mm
  MSL
                          L=7.68mm:
  MSTEP
        39
            40 W1=0.3mm
                          W2=5.0mm;
         40 41 W=5.0mm
                          L=7.42mm:
  MSL
  MSL
         21 43 W=0.38mm L=3.82mm;
  MTEE
         43
            44 45 W1=0.3mm W2=0.3mm W3=0.3mm:
            46 W=0.3mm
  MSI.
         45
                          L=4.1mm;
  MBEND2 46
            47 W=0.3mm;
  MST.
            48 W=0.3mm
         47
                          L=4.1mm;
  MSTEP
        48
            49 W1=0.3mm
                          W2=5.0mm;
         49
            50 W=5.0mm
                          L=3.7mm;
  MRSTUB 35 W=0.3mm L=4.45mm ANG=130;
  MRSTUB 44 W=0.3mm L=2.3mm ANG=130;
  EXTRINSIC4 141 142 143 14 15
      RG=1.33301
                                      RS=5.04386
                      RD=0.888452
      CDS=0.0414509pF
                     GDS=0.00441929
                                       CX=100pF
      LG=0.160598nH
                      LD=5.3121e-06nH
                                      LS=0.0718402nH
      CGE=0.143109pF
                      CDE=0.0924559pF;
  FETC 141 142 143
      A0=0.0826627
                    A1=0.335942
                                    A2=0.367757
                                                    A3=0.00858573
      GAMMA=1.86239 BETA=0.121412
                                    VDS0=0.742967
                                                    IS=5.26136e-11
      N=3.28559
```



```
Tau=1.0947ps Gmin= 0.841032e-12;
   VGS=-1.2;
   VDS=3;
   IND
                411 L=1000nH;
           50
   IND
               501 L=1000nH;
   VSOURCE 411 0 NAME=B_VGS VDC=VGS;
   VSOURCE 501 0 NAME=B VDS VDC=VDS;
   PIN = 9dBm;
   PORT.in 1 0 P[1]=PIN R=50;
          30 0 NAME=OUT R=50;
  CIRCUIT;
  Pout[0:N_SPECTRA] = if (PWout > 0) (10 * log10(PWout) + 30) else (NAN);
   Vs: sqrt(400 * 10^((Pin - 30)/10));
  MVs[0:N\_SPECTRA] = [0 Vs 0 0 0];
  PVs[0:N\_SPECTRA] = 0;
   Conversion Gain = POUT[2] - PIN;
End
Sweep
  HB: FREQ: 7GHZ Pin: from -3dBm to 16dBm step=1dBm
       Pout Conversion Gain MVout PVout MVs PVs
       {Xsweep title="Output Power Versus Input Power at 7GHz"
       Y=Pout[1].green & Pout[2].red & Pout[3].yellow & Pout[4].pink
       NXticks=10 Ymin=-60 Ymax=20 NYticks=8}
       {Xsweep title="Conversion Gain Versus Input Power at 7GHz"
       Y=Conversion_gain.green NXticks=10 Ymin=-50 Ymax=10 NYticks=6}
       {Waveform Title="Frequency Doubler Source and Output Voltage Waveforms"
       Spectrum=(MVs, PVs)."Vs(t)" & (MVout, PVout)."Vout(t)"
       Tmin=0 Tmax=0.2 NT=150 Ymin=-2 Ymax=2 NYTicks=4 pin=9};
  HB: FREQ: from 6.5GHZ to 8GHZ step 0.1GHZ
      Pin: from -3dBm to 16dBm step=1dBm
       Pout Conversion_Gain
       {Xsweep title="Output Power Versus Frequency at 9 dBm Input Power"
       Y=Pout[1].green & Pout[2].red & Pout[3].yellow & Pout[4].pink
       NXticks=6 Ymin=-50 Ymax=20 NYticks=7 Pin=9}
       {Xsweep title="Conversion Gain Versus Frequency at 9 dBm Input Power"
       Y=Conversion_Gain.green NXticks=6 Ymin=-17 Ymax=7 NYticks=6 Pin=9}
       {Visual Z=Conversion_Gain Z_title="CG" Zmin=-60 Zmax=4 Lines=ON
       Frame=OFF Paint=OFF Smooth=ON}
End
```